

# Motorola Semiconductor Application Note

---

## AN1775

### Expanding Digital Input with an A/D Converter

By **Brad Bierschenk**  
Motorola Applications Engineering  
Austin, Texas

#### Introduction

---

This application note documents a method of extending digital input using the analog-to-digital converter (ADC) of a microcontroller unit (MCU).

Many MCU applications require digital input and arbitration. For example, determining which key of a keypad was pressed. This is commonly done by arranging switches in a matrix configuration, connecting to a series of digital input pins, and reading a digital input data register to determine which key was pressed. While this method is easily implemented, it does require the use of an MCU's parallel port pins.

Some applications require all available bidirectional or input-only pins for other purposes. In such a case, an alternate method of arbitrating keypresses is desired. By using the ADC of an MCU connected to a resistor ladder, user input can be more efficiently processed.



## Background


---

### Dedicated Input

A microcontroller typically receives user input through digital input pins. The simplest implementation is a single switch directly connected to a digital input pin. This is easy to realize, but is not the most efficient use of resources, with one pin dedicated to one input. One port data bit represents the state of one switch.

### Matrix Input

Another method uses a keypad, a common element in embedded systems. These are ordinarily arranged in a matrix, as shown in [Figure 1](#). In this case, the byte value of an entire port data register can be polled to determine which key was pressed. This is more efficient, as a 4 x 4 keypad can interface 16 keys with eight input pins.

 


**Figure 1. Resistor Matrix Keypad Using Parallel Port Pins**

## ADC Alternative

In many cases, input pins are at a premium. One can't always freely assign input pins to the function of user input. A more efficient use of microcontroller resources can be devised. One common feature of many Motorola MCUs is the analog-to-digital converter, or ADC.

The ADC of a Motorola MCU usually features four to eight channels of analog input, which is compared with a reference voltage and converted to an 8-bit digital value. When a resistor ladder is connected to an analog input through switches in each segment, the conversion result can be used to arbitrate an input. This allows many keys to be interfaced with one input pin, with only a little more software overhead. **Figure 2** shows such an implementation.

 

**Figure 2. Resistor Ladder Keys Using an Analog Input Pin**

## Implementation

### ADC Operation

An MCU ADC typically has 8-bit *precision*. This means there are  $2^8$ , or 256, distinguishable A/D inputs, including 0. The analog inputs are converted to a binary number, which represents the magnitude of the input voltage in relation to a reference voltage.

The *range* of an ADC is the difference between its high and low reference voltages. This means an analog input between  $V_{REFH}$  and  $V_{REFL}$  will convert to an 8-bit number, with  $V_{REFL}$  converting to \$00 and  $V_{REFH}$  converting to \$FF.


The *resolution*, defined as the range divided by the precision, defines the analog step that a change in one least significant bit (LSB) represents.

In the case of a 5-volt, 8-bit ADC, the resolution is  $5/255$  (volts), or 19.6 mV. This means that a change in one LSB in the ADC data register reflects a change of about 20 mV at the analog input.

## Resistor Ladder Voltage Divider

Consider a resistor ladder connected to an ADC input, as shown in **Figure 3**. Because this arrangement is a voltage divider, each segment in the ladder can alter the voltage at the input when grounded. If switches are provided at each segment, one can selectively ground that segment, altering the composition of the divider, and thus altering the voltage presented to the ADC pin.

In this way, software can determine which switch in the ladder was selected by reading the resulting A/D data value. The resistor  $R_0$  acts as a pullup to maintain  $V_{DD}$  on the analog input line while no keys are active. Thus, a conversion value of \$FF indicates that no key has been pressed.

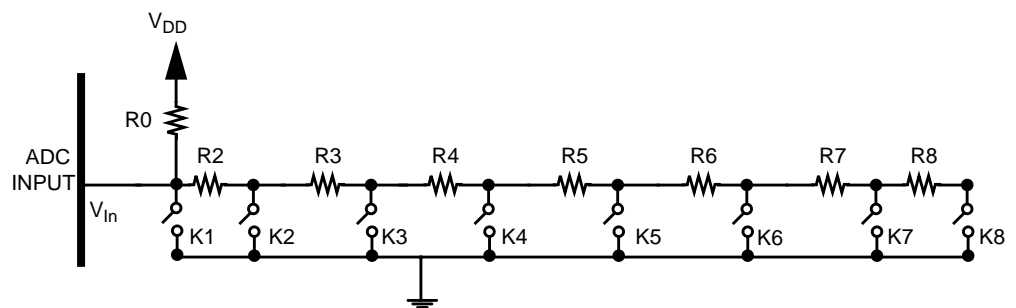

**Figure 3. Digital Input Alternative**

**Considerations** Using this method, one can theoretically connect 255 input switches to one ADC pin. However, there are many potential sources of inaccuracies, which make it impractical to connect so many key inputs. One should account for some error padding.

**Resistor Precision** One inaccuracy is provided by the resistors themselves. Resistors are categorized according to their variance from a labeled value. The application should be tolerant to the precision of the resistors being used (typically, 1 percent or 5 percent). Also, a calculated resistor value might not be a commonly available value, so the user should plan for a range of resistor values.

**ADC Accuracy** Typically, an 8-bit ADC is accurate within two least significant bits. This should be accounted for as well. The best way to allow for these tolerances is to assign to each key switch a range of resulting A/D data register values.

If an analog input falls within a particular range, one can determine that the key was pressed. By adjusting the range of ADC results which represent a given keypress, the user can change the error margin for the application.

To ensure the best ADC accuracy, the full range of the converter should be used. In cases where the high reference is not variable, it is typically fixed at the operating voltage.


A spreadsheet is a good way to determine resistor values and A/D result ranges. An example of computing values for [Figure 3](#) are shown in [Table 1](#).

**Table 1. Spreadsheet Calculations**

$V_{DD} =$	5	Converter Resolution =		0.01961	(V <sub>DD</sub> /255)			
# Keys =	8							
Voltage Steps =	0.625	(V <sub>DD</sub> /# Keys)	R0 =	10000	(Pullup)			
							(Hex)	(Hex)
Key pressed	$V_{In}$	Req	Rn		Vinmin	Vinmax	ADDRmin	ADDRmax
No Key	5	0	10000		4.6875	5	EF	FF
1	0	0	0		0	0.3125	0	F
2	0.625	1429	1429		0.3125	0.9375	F	2F
3	1.25	3333	1904		0.9375	1.5625	2F	4F
4	1.875	6000	2667		1.5625	2.1875	4F	6F
5	2.5	10000	4000		2.1875	2.8125	6F	8F
6	3.125	16667	6667		2.8125	3.4375	8F	AF
7	3.75	30000	13333		3.4375	4.0625	AF	CF
8	4.375	70000	40000		4.0625	4.6875	CF	EF

Some notes on the spreadsheet:

- $V_{In}$  is determined by decrementing the high voltage reference by the voltage step for each segment in the ladder. (See [Figure 4](#).)
- Rn is the resistor value of the current key segment needed to form desired equivalent resistance Req.
- Req represents the equivalent resistance of ladder, including the current resistor (Rn) and excluding the pullup resistor (R0).
- Vinmin and Vinmax are the minimum and maximum voltages that can be arbitrated as a particular key. In this case,  $V_{In} \pm V_{step}/2$  was used.
- ADDRmin and ADDRmax are the ADC data register value range used to represent a given keypress. This range can be narrowed or widened to affect precision. In this case, the ranges were maximized, so no conversion result is undefined.
- This particular spreadsheet did not use resistor precision, but this could be considered to further pad the error.

 

**Figure 4. Voltage Divider**

### Constants

First,  $V_{DD}$  (or  $V_{REFH}$ , the high reference for the converter) and the number of keys are determined. The converter resolution is found by dividing  $V_{DD}$  by the converter precision. The number of voltage steps needed is  $V_{DD}$  divided by the number of key switches. An ADC should always be operated at its full range. The pullup resistor,  $R_0$ , typically, should be chosen between 4.7 k (to limit current) to 22 k (to limit time constant).

### Variables

Once these constant values are decided, a spreadsheet can be used to determine the resistor values needed in each segment of the divider ladder, according to the desired input voltages.

When using an ADC, always use the entire range of the converter ( $V_{REFH} - V_{REFL}$ ). This is the reason for determining the voltage steps first ( $V_{DD} - n \cdot \text{step value}$ ) and then calculating the necessary resistor values to achieve these voltages through the divider.

For each segment in the ladder, the  $n^{\text{th}}$  segment's necessary resistor value needs to be calculated ( $R_n$  in the spreadsheet). When a key is pressed, the equivalent resistance of the included segment resistors forms a voltage divider with the pullup resistor.

Given the voltage desired at the ADC input ( $V_{In}$ ), the user can determine the equivalent resistance needed to achieve that voltage by:

$$Req(n) = (V_{In} \cdot R_0) / (V_{REFH} - V_{In})$$

The resistor that will form the needed equivalent resistance with the other resistors in the ladder can be determined, as:

$$R_n = Req(n) - Req(n - 1)$$

The only exception is key 1, which connects  $V_{SS}$  to the ADC input and needs no resistor.

By assigning a range of ADC conversion values to each key, the user can provide a fair amount of error padding. Considerations include resistor tolerance, ADC accuracy, and parasitic time constants. The range of conversion values for a particular keypress can be narrowed to improve the accuracy of the application. Or, for “quick and dirty” arbitration, keep the range as wide as possible.

### Using a Single Resistor Value

The method presented here used different resistor values to produce equal voltage intervals. Another method would be to use the same resistance value for all segments in the divider. The disadvantage of using the same resistor values is that it greatly diminishes the effective range of conversions. Also, if resistances are kept equal, the voltage step between switches approaches the resolution of the ADC. Therefore, the error margin diminishes as more keys are added.

### Programming Considerations

There are several ways to implement such an application. One thing to choose is whether to poll the ADC when desired or link a keypress to an interrupt source.

Some ADCs continuously convert once enabled, allowing a new value to be available every 32 clock cycles. Others do a single conversion when a register is written to and don't do another conversion until the register is written to again.

A polling scheme can use a periodic timing source as a signal to poll. For example, the real-time interrupt (RTI) or timer overflow (TOF) interrupt can be used to scan the ADC input at a given rate.

Not linking a keypress to an interrupt source can cause timing problems and might miss a keypress. Careful consideration should be given to timing and voltage error requirements to determine if this method is appropriate.



## A Brief Example with the MC68HC705P6A MCU

---

The small code segment example that follows illustrates the software implementation of this method of keypress arbitration. The example was defined around the spreadsheet analysis example shown in [Table 1](#).

The MC68HC705P6A (P6A) MCU features a 4-channel, 8-bit A/D converter. The P6A ADC uses continuous conversion, making a new value available every 32 internal clock cycles after being turned on.

The software example assumes a resistor ladder is connected to ADO (A/D channel 0, port C, pin 6). The software is not intended to be a complete application.

This software starts the ADC, selects channel 0 for A/D conversions, then polls the ADC data register to determine if a key was pressed. The software uses a lookup table, with predefined maximum and minimum ADC values which represent a specific segment in the divider being grounded.

Once the key has been arbitrated, the RAM variable InKey will tell an application which key was switched most recently.

## Code Listings

---

```
* -----
* EXPANDIO.ASM
* Written for the MC68HC705P6A microcontroller
* A code segment example to illustrate the use of the A/D
* converter for key input arbitration
*
* This simple example polls the AD0 channel, compares the
* conversion result to a lookup table, and determines
* which of 8 keys were pressed.
* -----

; Memory map equates
RAMSPACE      EQU      $50
ROMSPACE      EQU      $100

; A/D Registers
ADC           EQU      $1D           ;A/D Data register
ADSC         EQU      $1E           ;A/D Status and control

; ADSC Bits
CC           EQU      7             ;Conversion complete flag
ADRC        EQU      6             ;A/D RC oscillator enable
ADON        EQU      5             ;A/D enable bit

* -----
; RAM Variables
* -----
                ORG      RAMSPACE      ;Start of user RAM
InKey       RMB      1             ;Identifies the last key pressed
ADValue     RMB      1             ;Stores the last ADC result

* -----
; Program code
; Simply loops, polling the A/D converter channel AD0
; and determining which key was pressed
* -----
                ORG      ROMSPACE      ;Start of user ROM
Start:
                LDA      #$20           ;Turn on A/D, select AD0 channel
                STA      ADSC

MainLoop:
                BRCLR   CC,ADSC,*       ;Wait for conversion complete
                LDA      ADC             ;Get the result
                STA      ADValue        ;Record the result
                CLR     InKey           ;Clear the InKey variable
                CLRX    CLRX            ;Clear the offset
```

```
;Check the entries in the table, to find the ADC value range
;that corresponds to the ADC data register value.
```

```
KeyLoop:
```

```
    LDA    KeyTable+1,X        ;Check high range
    CMP    ADValue
    BLS    Match              ;Within range
    LDA    KeyTable,X         ;Check low range
    CMP    ADValue
    BLS    Match              ;Within range
    INCX                       ;Point to next table record
    INCX
    ;Increment the key value, when a match is made,
    ;the variable will contain the key that was pressed.
    INC    InKey
    BRA    KeyLoop
```

```
; At this point, InKey variable holds keypress information
; One can arbitrate the key press here. For this simple example
; we just repeat the main loop
```

```
Match:
```

```
    BRA    MainLoop
```

```
* -----
; Key lookup table. Holds the minimum and maximum ADC values
; which identify a particular key in the resistor ladder
* -----
```


```
KeyTable:
```

```
NoKey      FCB    $EF,$FF        ;No key pressed
Key1       FCB    $00,$0F
Key2       FCB    $0F,$2F
Key3       FCB    $2F,$4F
Key4       FCB    $4F,$6F
Key5       FCB    $6F,$8F
Key6       FCB    $8F,$AF
Key7       FCB    $AF,$CF
Key8       FCB    $CF,$EF
```

```
* -----
; Vector definitions
* -----
```

```
    ORG    $1FFE                ;Reset vector
    FDB    Start
```

# Application Note

Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters which may be provided in Motorola data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Motorola does not convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

## How to reach us:

**USA/EUROPE/Locations Not Listed:** Motorola Literature Distribution, P.O. Box 5405, Denver, Colorado 80217, 1-800-441-2447 or 1-303-675-2140. Customer Focus Center, 1-800-521-6274

**JAPAN:** Nippon Motorola Ltd.: SPD, Strategic Planning Office, 141, 4-32-1 Nishi-Gotanda, Shinagawa-Ku, Tokyo, Japan. 03-5487-8488

**ASIA/PACIFIC:** Motorola Semiconductors H.K. Ltd., 8B Tai Ping Industrial Park, 51 Ting Kok Road, Tai Po, N.T., Hong Kong. 852-26629298

**Mfax™, Motorola Fax Back System:** RMFAX0@email.sps.mot.com; <http://sps.motorola.com/mfax/>;

TOUCHTONE, 1-602-244-6609; US and Canada ONLY, 1-800-774-1848

**HOME PAGE:** <http://motorola.com/sps/>

Mfax is a trademark of Motorola, Inc.



**MOTOROLA**

© Motorola, Inc., 1998

AN1775/D